

# **BASIC ELECTRONICS(3320701)**

## **OSCILLATOR**

# Need of an Oscillator


- An oscillator circuit is capable of producing ac voltage of desired frequency and waveshape.
- To test performance of electronic circuits, it is called **signal generator**.
- It can produce square, pulse, triangular, or **sawtooth waveshape**.
- High frequency oscillator are used in broadcasting.
- **Microwave oven** uses an oscillator.
- Used for **induction heating** and **dielectric heating**.

# Types of Oscillators

- Sinusoidal or non-sinusoidal.
- An oscillator generating square wave or a pulse train is called **multivibrator** :
  1. Bistable multivibrator (Flip-Flop Circuit).
  2. Monostable multivibrator.
  3. Astable multivibrator (Free-running).
- Depending upon type of feedback, we have
  1. Tuned Circuit (*LC*) oscillators.
  2. *RC* oscillators, and
  3. Crystal oscillators.

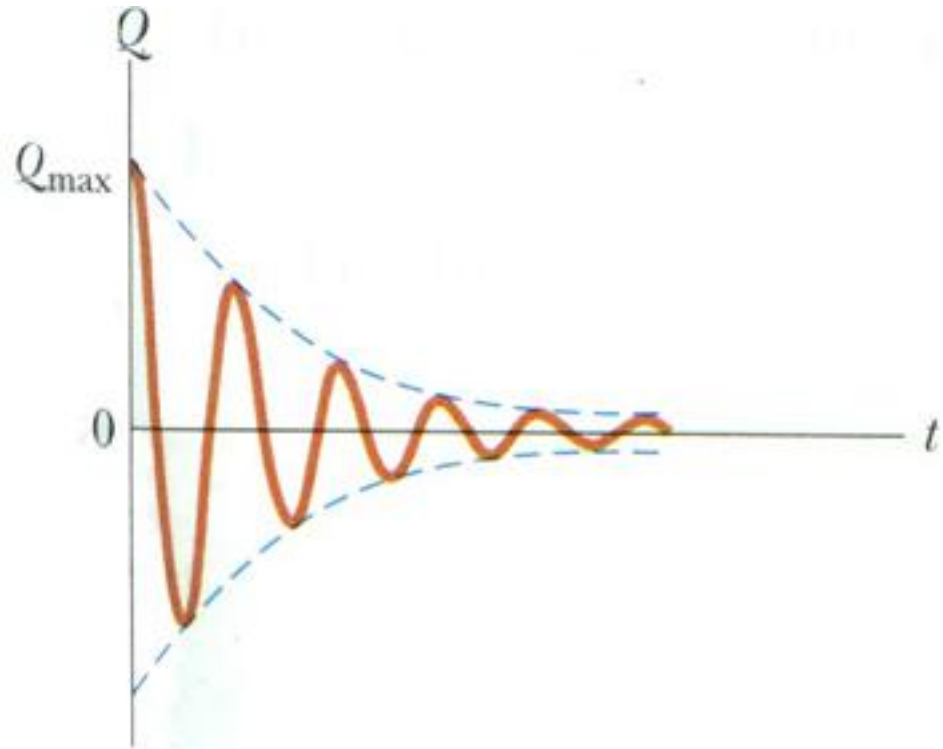
# Damped oscillation


➤ WHEN THE  
MAGNITUDE OF  
VOLTAGE IS  
DECREASING &  
AFTER SOME TIME,  
IT BECOMES  
0(ZERO)  
OSCILLATION  
STOPPED.


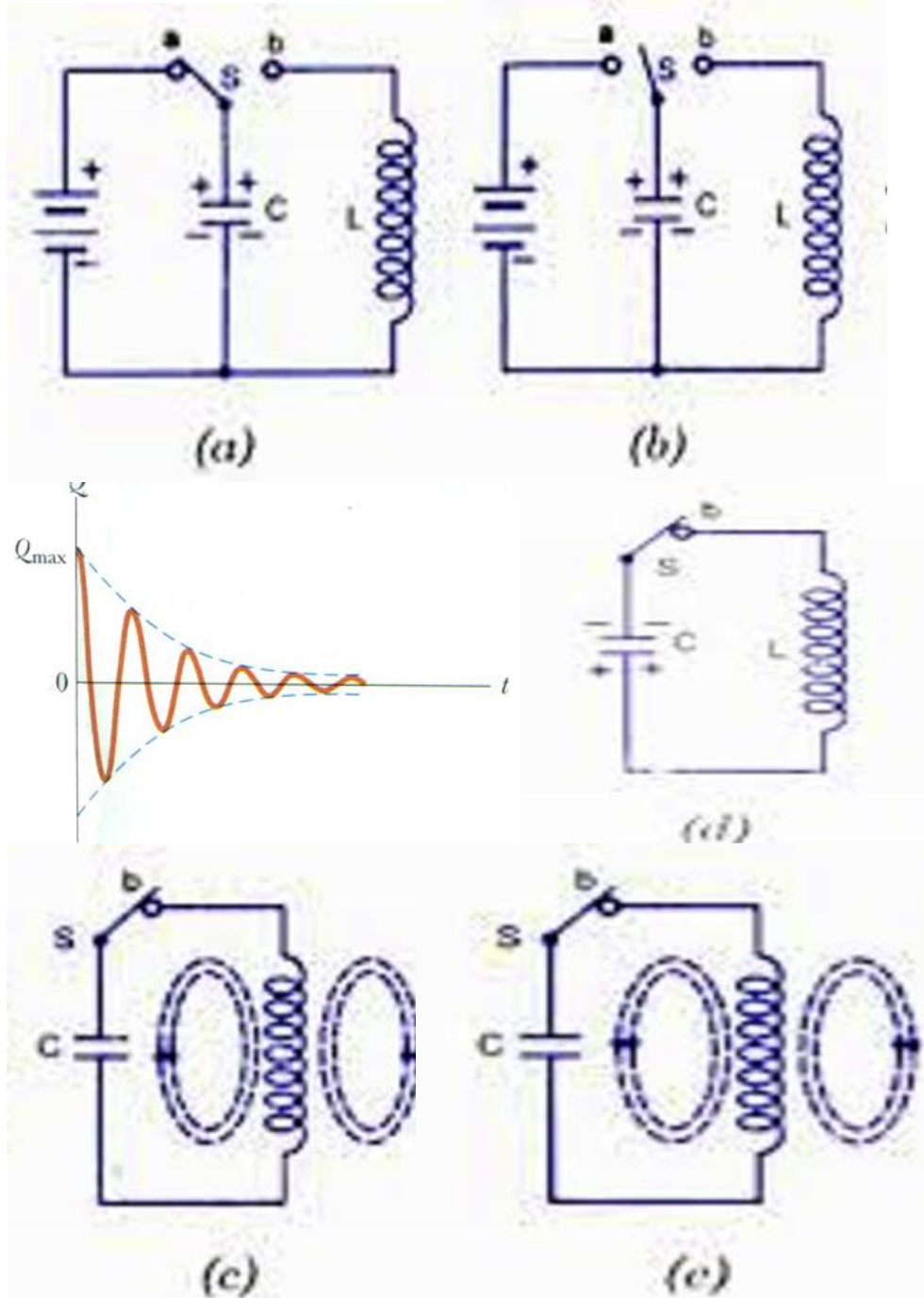
# DAMPED OSCILLATION IN LC TUNED CIRCUIT

- IN FIG A SHOWN THAT KEY S IS BROUGHT TO POSITION A. THE CAPASITOR C CHARGES. SO POSITIVE CHARGE IS TO UPPER PLATE W.R.T BOTTOM PLATE. SO VOLTAGE INCREASES & ENERGY STORED.
- NOW WHEN KEY S IS CONNECTED TO POSITION C CAPACITOR CONNECTED TO L. SO VOLTAGE DECREASES. SO DAMPED OSCILLIATION IS DONE.



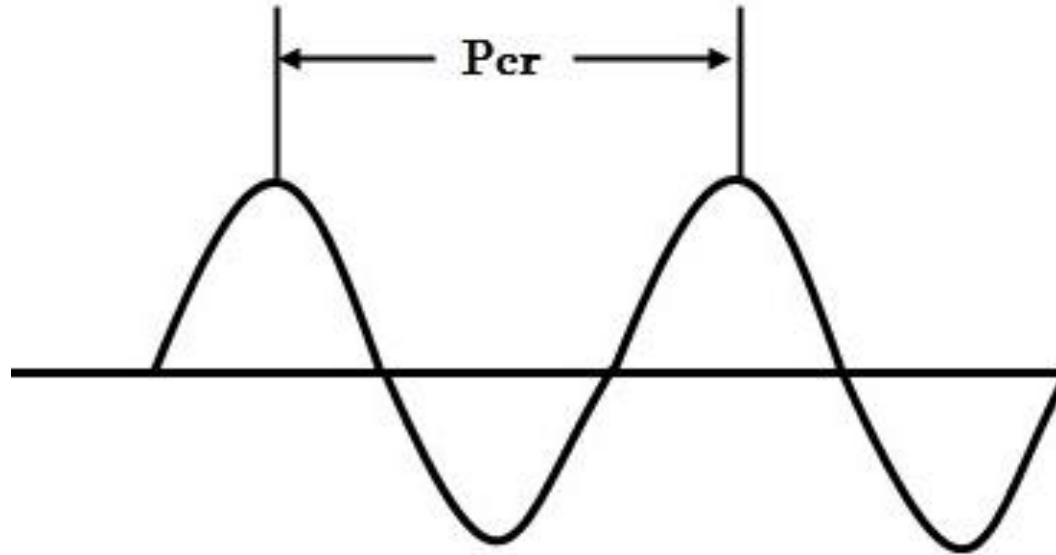


Sustained Oscillations  
with period  $Per$

## SUSTAINED OSCILLATION

WHEN PRODUCED ENERGY IS EQUAL TO WASTE ENERGY  
IN CAPACITOR & INDUCTOR.
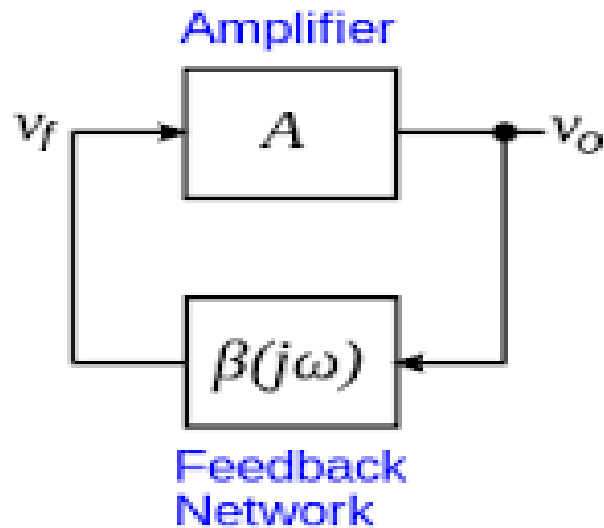
# AMPLIFIER WITH POSITIVE FEEDBACK AS OSCILLIATOR



IN FIGURE POSITIVE FEEDBACK SHOWN .A IS GAIN . POSITIVE FEEDBACK IS GIVEN TO B.

TOTAL GAIN :-  $A_f = A / (1 - AB)$

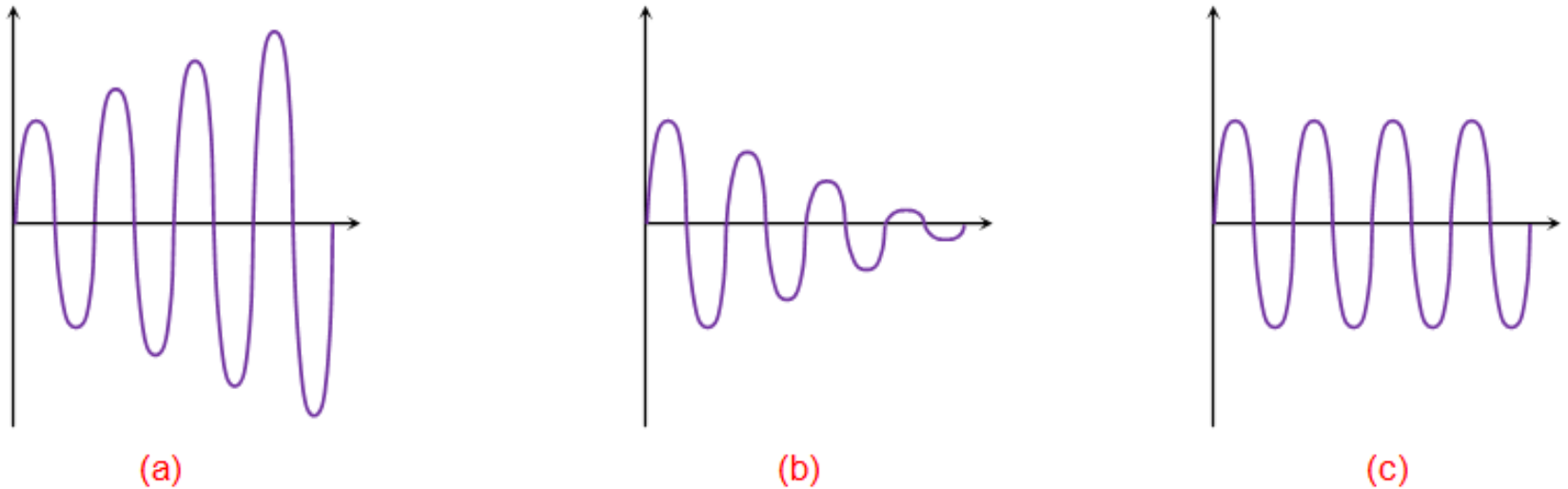


Figure 2 (a) Increasing Oscillations (b) Decaying Oscillations (c) Constant-Amplitude Oscillations

❑ IF  $AB < 1$  SO  $V_f$  DECREASES (fig.b)

❑ IF  $AB > 1$  SO  $V_f$  INCREASES (fig.a)

❑ IF  $AB = 1$  (fig.c)

$$A_f = \frac{A}{1-AB} = \frac{1}{0} = \text{Infinite.}$$



# REQUIRMENT OF AN OSCILLIATOR

- ACTIVE DEVICE:-It works as amplifier. For this value/FET/transistor are used.
- POWER SUPPLY:-It is necessary for biasing the active device & to compensate for the energy loss.
- FREQUENCY DETERMINING NETWORK:-In LC oscillation frequency of oscilliator depends upon the tuned circuit.


# REQUIRMENT OF OSCILLIATOR

- POSITIVE FEEDBACK:- It is essential.
- Initially value of  $AB$  should be more than 1.
- Value of loop gain  $AB$  should be equal to 1 after the oscillations are started.

# Hartley Oscillator

- The **Hartley oscillator** is an electronic oscillator circuit in which the oscillation determined by a tuned circuit consisting of **capacitors & inductors** , that is , an **LC oscillator**. The circuit was invented in 1915 by **American** engineer **Ralph Hartley**.
- The distinguishing feature of the Hartley oscillator is that the tuned circuit consist of a **single capacitor** in **parallel with two inductors in series**, and the **feedback signal** needed for oscillation is **taken** from the **center connection of two inductors**.

# The diagram of Hartley oscillator

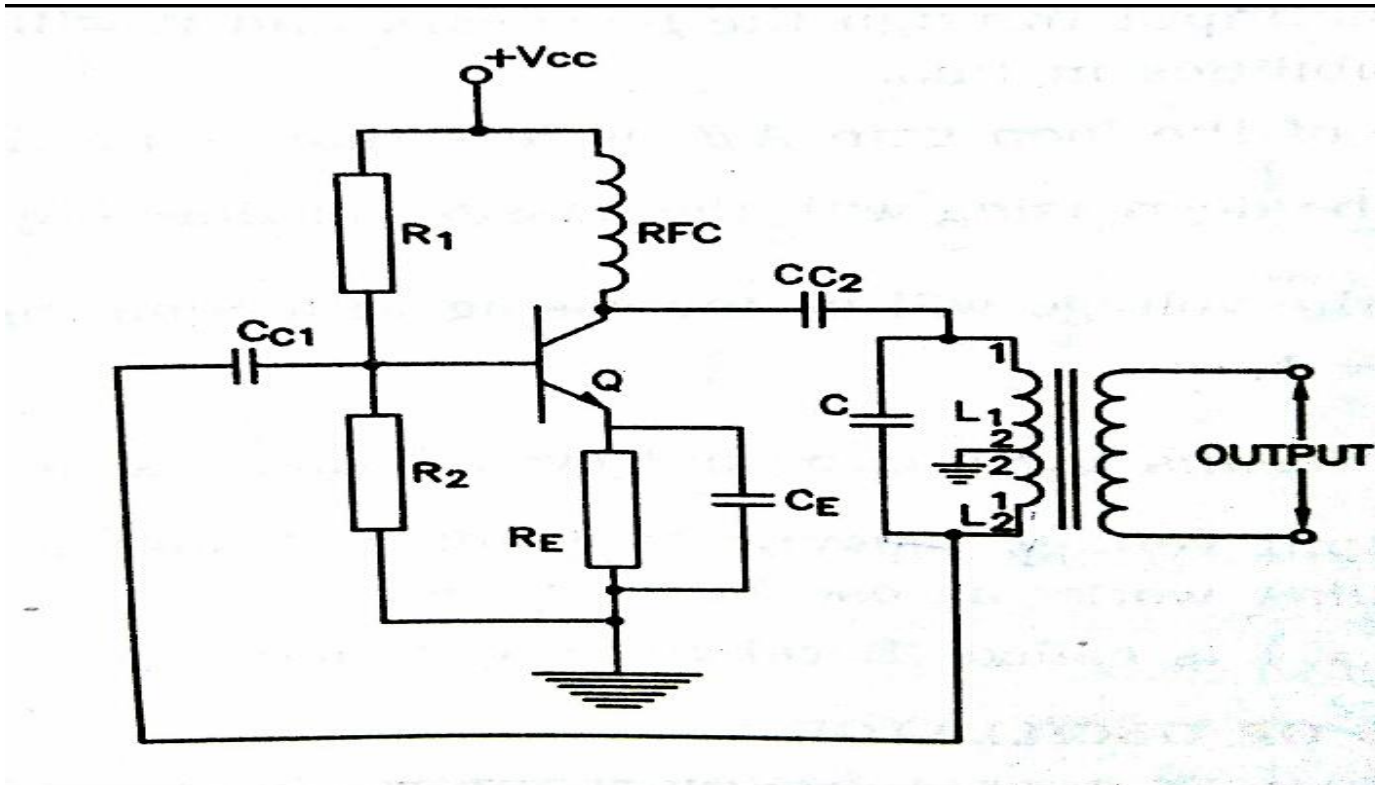

# Hartley Oscillator

- Some important formulae from Hartley oscillator:


$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$L = L1 + L2$$

# Colpitt Oscillator

- A Colpitt oscillator, invented in 1918 by American engineer Edwin H. Colpitts, is one of a number of designs for LC oscillators, electronic oscillator that use a combination of inductors and capacitors to produce an oscillation at a certain frequency.
- The distinguishing feature of the colpitts oscillator is that the feedback for the active device is taken from a voltage divider made of two capacitors in series across the inductor.

# The diagram of Colpitt oscillator

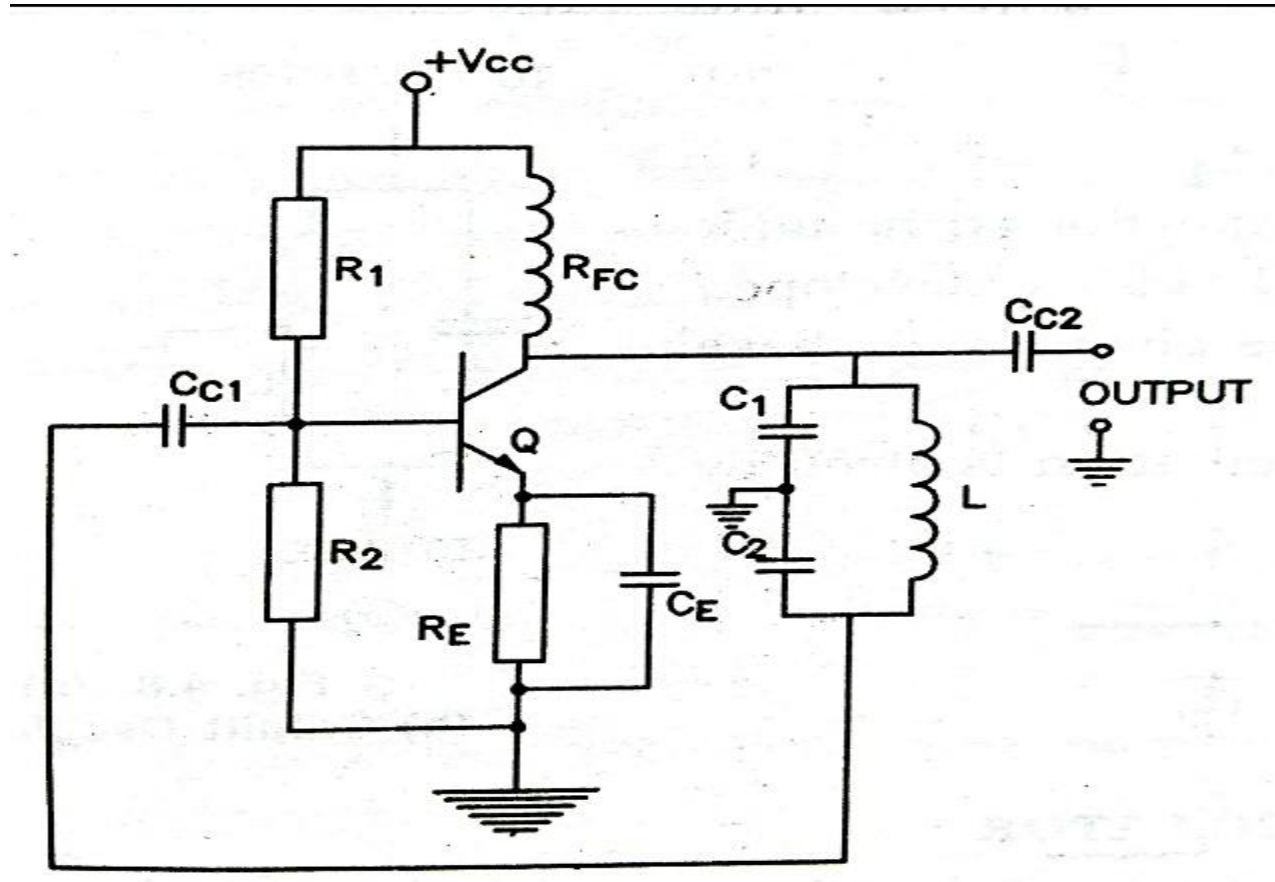

# Colpitt Oscillator

- Some important formulae from colpitt oscillator:


$$f = \frac{1}{2\pi\sqrt{LC}}$$

$$C = \frac{C_1 C_2}{C_1 + C_2}$$



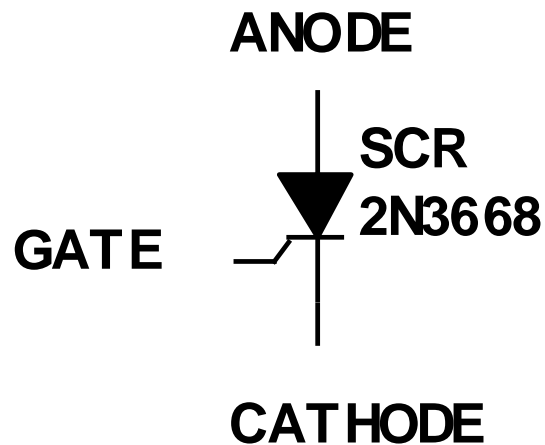
# Silicon Controlled Rectifier-SCR

- Circuit Symbol and Terminal Identification


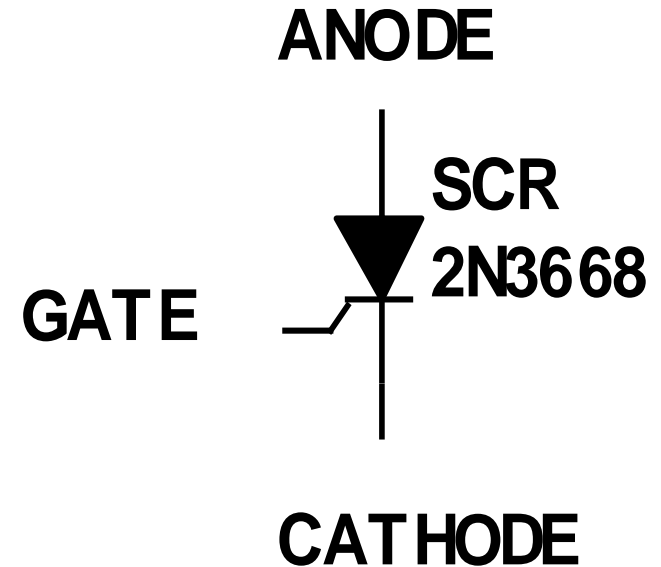
# SCR / Thyristor


- Anode and Cathode terminals as conventional pn junction diode
- Gate terminal for a controlling input signal




# SCR/ Thyristor

- An SCR (Thyristor) is a “controlled” rectifier (diode) Control the conduction under forward bias by applying a current into the Gate terminal Under reverse bias, looks like conventional pn junction diode.
- 4-layer (pnpn) device.
- Anode, Cathode as for a conventional pn junction diode.
- Cathode Gate brought out for controlling input.

# Equivalent Circuit

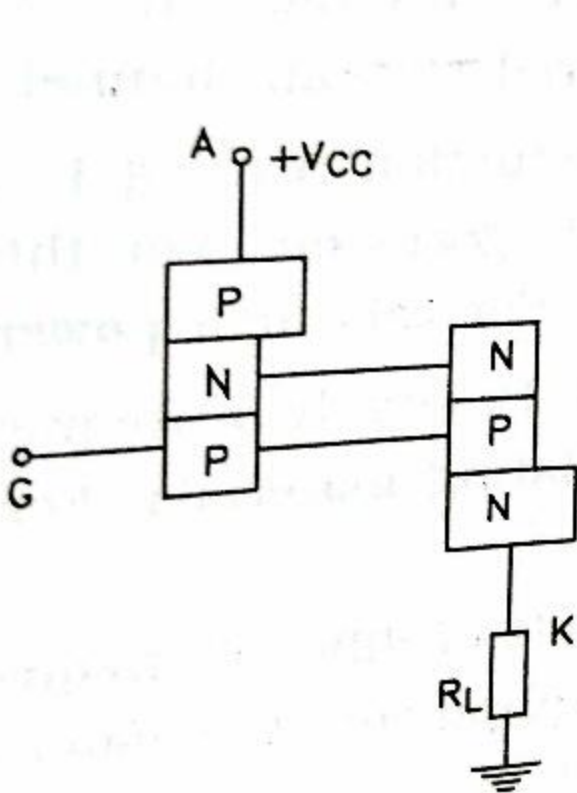


(a)

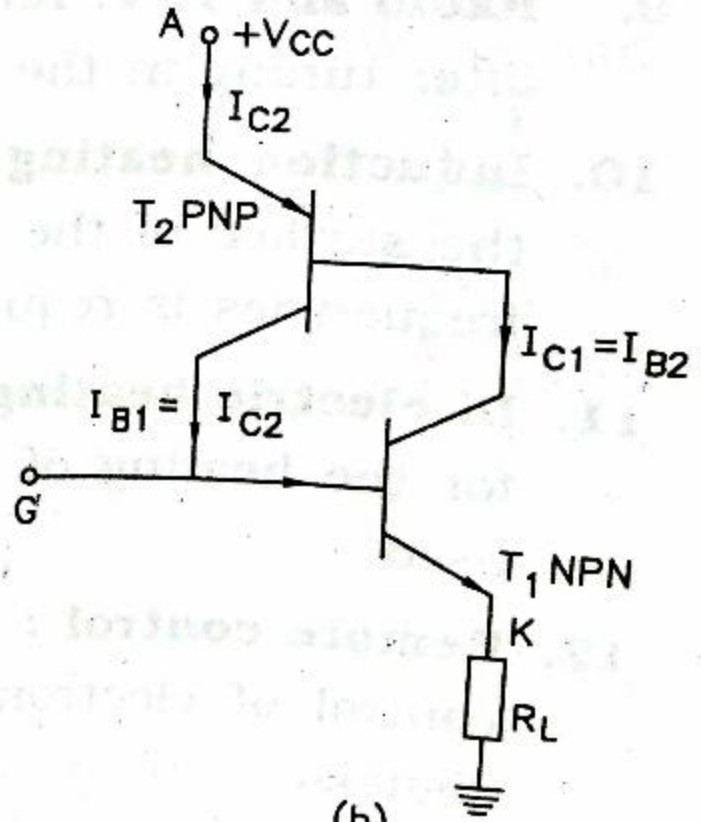

(b)

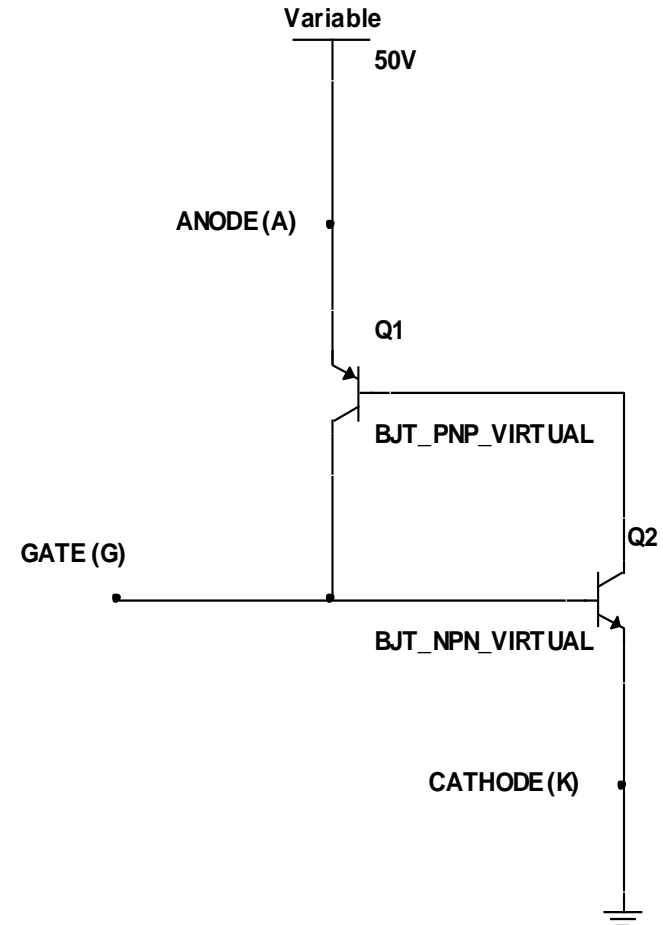
# Apply Biasing

- With the Gate terminal OPEN, both transistors are OFF. As the applied voltage increases, there will be a “breakdown” that causes both transistors to conduct (saturate) making  $I_F > 0$  and  $V_{AK} = 0$ .
- $V_{Breakdown} = V_{BR(F)}$


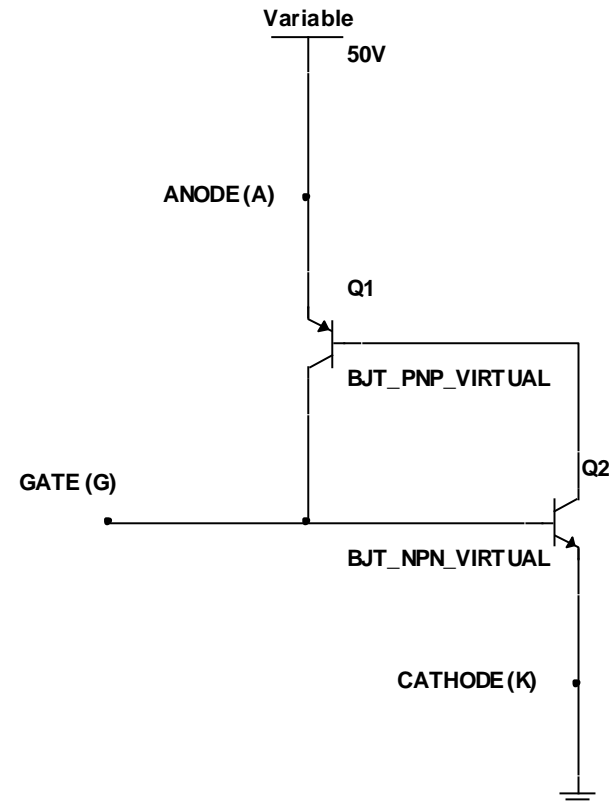
# Apply a Gate Current

- For  $0 < V_{AK} < V_{BR(F)}$ ,
- Turn  $Q_2$  ON by applying a current into the Gate
- This causes  $Q_1$  to turn ON, and eventually both transistors SATURATE
- $V_{AK} = V_{CEsat} + V_{BEsat}$
- If the Gate pulse is removed,  $Q_1$  and  $Q_2$  still stay ON!



# How do you turn it OFF?

- Cause the forward current to fall below the value of the “holding” current,  $I_H$
- Reverse bias the device.

# Application Of SCR

- It is used for the speed control of the D . C motors.
- It used for the temperature control of the furnace,
- It is used in electronic ignition of automobiles.
- It is used in poly phase rectifiers and inverter.



**THANK YOU**