

**GUJARAT TECHNOLOGICAL UNIVERSITY**  
**DIPLOMA ENGINEERING – SEMESTER – I EXAMINATION –WINTER - 2018**

**Subject Code:3310702****Date: 09-01-2019****Subject Name: Fundamental Of Digital Electronics****Time:10:30 AM TO 01:00 PM****Total Marks: 70****Instructions:**

1. Attempt all questions.
2. Make Suitable assumptions wherever necessary.
3. Figures to the right indicate full marks.
4. Use of programmable & Communication aids are strictly prohibited.
5. Use of only simple calculator is permitted in Mathematics.
6. English version is authentic.

<b>Q.1</b>	Answer any seven out of ten. દરેક પણ સાત ના જવાબ લખો.	<b>14</b>
	1. $(557)_8 = ( )_2 = ( )_{16}$	
	2. Define: Analog signal, Digital signal	
	3. What is difference between 1's complement and 2's complement?	
	4. Define: MSB, LSB.	
	5. Draw the truth table for NOT GATE and EX-OR GATE.	
	6. Differentiate between Min term and Max term	
	7. Draw the symbol for AND GATE and OR GATE	
	8. Find 9's Complement of 4069.	
	9. What is SOP?	
	10. De-Morgan's theorems	
<b>Q.2</b>	(a) State and Prove De-Morgan's theorems.	<b>03</b>
<b>પ્રશ્ન ૨.</b>	(અ) De-Morgan's theorems લખો અને સાચીત કરો.	<b>03</b>
	OR	
	(a) Weighted Binary code ? explain any one.	<b>03</b>
	(અ) Weighted Binary code શું છે ? કોઈ પણ એક સમજાવો.	<b>03</b>
	(b) Draw the logic circuit using NAND gates for the Boolean expression $A = XY' + X'Y + Z$	<b>03</b>
	(અ) Boolean expression $A = XY' + X'Y + Z$ માટે NAND gatesનો ઉપયોગ કરી logic circuit દોરો.	<b>03</b>

	OR	
(b)	Explain EX-NOR gate With Truth table.	03
(ચ)	Truth table સાથે EX-NOR gate સમજાવો.	03
(c)	Draw and explain 4-bit parallel subtractor.	04
(ક)	4-bit parallel subtractor દોરો તથા સમજાવો.	04
	OR	
(c)	Draw and explain full adder.	04
(ક)	ફૂલ એડર દોરો તથા સમજાવો.	04
(d)	Explain Commutative and Associative laws for Boolean algebra.	04
(સ)	Boolean algebra માટે Commutative તથા Associative laws સમજાવો.	04
	OR	
(d)	Give difference between sequential and combinational circuits.	04
(સ)	sequential તથા combinational circuits વચ્ચેનો તફાવત આપો.	04
<b>Q.3</b>	(a) Explain half subtractor with circuit and truth table	03
<b>પ્રશ્ન 3</b>	(ચ) Half subtractor સર્કિટ તથા truth table સાથે સમજાવો.	03
	OR	
(a)	Explain full subtractor with circuit and truth table.	03
(ચ)	Full subtractor સર્કિટ તથા truth table સાથે સમજાવો.	03
(b)	Design AND gate using NOR gate.	03
(ક)	NOR gate ની ઉપયોગ કરીને AND gate બનાવો.	03
	OR	
(b)	Differentiate POS and SOP.	03
(ચ)	POS તથા SOP વચ્ચેનો તફાવત આપો.	03
(c)	Draw and explain 8:1 multiplexer.	04
(ક)	8:1 multiplexer દોરો તથા સમજાવો.	04
	OR	
(c)	Using K-map build logic circuit for full adder.	04
(ક)	K-map વાપરીને ફૂલ એડર ની logic circuit બનાવો.	04
(d)	Explain don't care condition with example.	04
(સ)	Don't care condition ઉદાહરણ સાથે સમજાવો.	04
	OR	
(d)	Compare Half adder and Full adder.	04
(સ)	Half adder તથા Full adder ની સરખામણી કરો.	04
<b>Q.4</b>	(a) What is demultiplexer ? Explain 1:4 demultiplexer.	03
<b>પ્રશ્ન 4</b>	(ચ) Demultiplexer શું છે ? 1:4 demultiplexer સમજાવો.	03
	OR	
(a)	What is decoder ? Explain 2:4 decoder	03
(ચ)	Decoder શું છે ? 2:4 decoder સમજાવો.	03
(b)	Draw logic circuit for following Boolean Expression.	04
(i)	$Y = AB + AC' + A'BC$	
(ii)	$Y = (A' + B + C)(A + B' + C)$	
(ચ)	નીચેની Boolean Expression માટે logic circuit દોરો.	04
(i)	$Y = AB + AC' + A'BC$	
(ii)	$Y = (A' + B + C)(A + B' + C)$	

OR

- (b) Reduce following function using K-Map 04  
 $F(A,B,C,D) = \pi(0,1,2,4,6,8,9,10,11,12,13)$

(c) K-Map નો ઉપયોગ કરીને ફક્ત ક્રિયાના રૂપમાં  $F(A,B,C,D) = \pi(0,1,2,4,6,8,9,10,11,12,13)$  08  
 reduce કરો.

(d) Write SOP form for function  $F(A,B,C,D) = (A+B')(A+C')(A+B'+D)$ . 07

(e) Function  $F(A,B,C,D) = (A+B')(A+C')(A+B'+D)$  માટે SOP ફક્ત રૂપ દારવો. 09

  

(a) What is comparator? Explain 1-bit magnitude comparator. 04

(f) Comparator શું છે ? 1-bit magnitude comparator સમજાવો. 08

(g) What is encoder? Explain 8:3 encoder 04

(h) Encoder શું છે ? 8:3 encoder સમજાવો. 08

(i) Draw logic circuit for given expression using only NAND gates. 03  
 $Y = (A'+B').(A'+B'+C)$

(j) ફક્ત NAND gates નો ઉપયોગ કરીને expression  $Y = (A'+B').(A'+B'+C)$  માટે logic circuit દોરો. 03

(k) Explain serial and parallel register. 03

(l) Serial તથા parallel register સમજાવો. 03

\*\*\*\*\*